

# ELECTRICITY

# 101


a very basic review

Richard S. Reines

Senior Electrical Engineer

Public Service Commission of  
Wisconsin
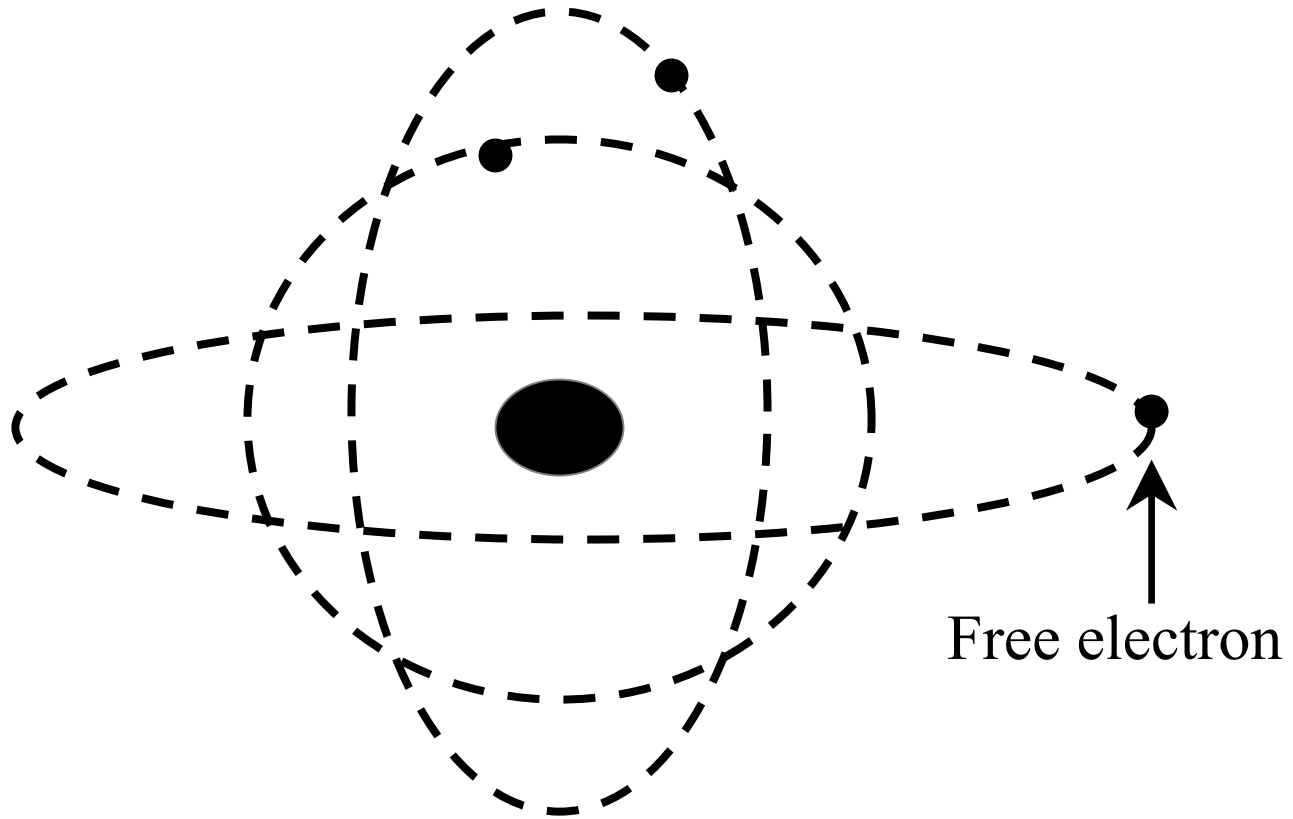
# The basis for electricity – the atom with its electron “cloud”.



# CONDUCTORS / SEMI- CONDUCTORS

ELEMENT	AL	FE	CU	AG	AU	C	SI	GE
ATOMIC #	13	26	29	47	79	6	14	32
ATOMIC WT	27	56	63	108	197	12	28	72
<b>CONDUCTIVITY</b>	2.6	9.7	1.7	1.6	2.4	1400	85000	45
VALENCE	+3	+2	+1	+1	+1	±4	±4	±4

# Earth resistivities

Physical composition	Resistivity	Resistivity
	Ohm-cm	Ohm -meter
Sea Water	100 - 200	1 - 2
Marsh	200 - 300	2 - 3
Clay	300 - 16k	3 - 160
Clay, sand, gravel	1k - 135k	10 - 1.4k
Chalk	6k - 40k	60 - 400
Shale	10k - 50k	100 - 500
Sand	9k - 80k	90 - 800
Sand, gravel	30k - 500k	300 - 5k
Rock	50k - 1m	500 - 10k

# **Range: Conductors to insulators**

- **Conductors: metals with crystalline structure and “free” electron cloud.**
- **Ionized gasses.**
- **Semiconductors - ‘tailor-made’ conductivity.**
- **Insulators: barely perceptible conductivity.**
- **A vacuum is the perfect insulator, yet a stream of electron particles and electromagnetic waves can travel through it.**

# Electricity: an energy transfer medium

- **FLOW: Source → conduction medium → load  
conduction medium back to source.**
  - A COMPLETE CIRCUIT
  - OBEYS THE 'CONSERVATION OF ENERGY' LAW
- **Flow of electrons vs. flow of normal current**
  - Ben Franklin GOT IT WRONG!
  - ELECTRONS FLOW FROM A – SOURCE TO A + SINK, NORMAL CURRENT FLOW IS VICE VERSA

# Two 'types' of electricity

- **Direct Current (DC)**
  - Steady on or off characteristic
  - A battery
  - Static discharge
  - Lightning
- **Alternating Current (AC)**
  - Changes repeatably with time at some characteristic frequency
  - Household power
  - Audio: speech, music
  - AM/FM radio, TV
  - Cell phone, satellite
  - Radar, microwaves

# Define “current”

- $\sim 6 \times 10^{18}$  (billion, billion) electrons per second past a single point = 1 Ampere of current.
- The symbol is ‘ I ’
- It flows – like water in a pipe
- 1 milliAmp (mA) = 1/1,000 Ampere
- 1 microAmp ( $\mu$ A) = 1/1,000 mA = 1/1,000,000 Ampere

# Define “voltage”



- **Very hard to define using basic units (1 Newton force exerted over 1 meter distance in 1 second = 1 Watt  
1 Watt / 1 Ampere = 1 Volt)**
- **Easier to have a ‘feel’ for voltage levels 1.5 v. battery, 9 v. battery, 12 v. battery, 120 v rms house system, etc.**
- **Voltage is a pressure pushing electrons to form a current. It is like “head” in a water system or the height of a waterfall.**
- **The symbol is ‘ V ‘**

# Define “resistance”


- **1 Volt/1 Amp = 1 Ohm**
- **Is like the diameter of a water pipe – small diameter (greater resistance) means less flow is possible, larger diameter (less resistance) means greater flow is possible.**
- **For a given diameter pipe (fixed resistance), increasing the pressure (voltage) will increase the water flow (current).**
- **Symbol is R**
- **Range of practical resistance values is very large**
  - **micro-ohms, milli-ohms, ohms, kilo-ohms, mega-ohms, giga-ohms.**
- **Can be lumped or distributed**

# Fields

voltage = X v.

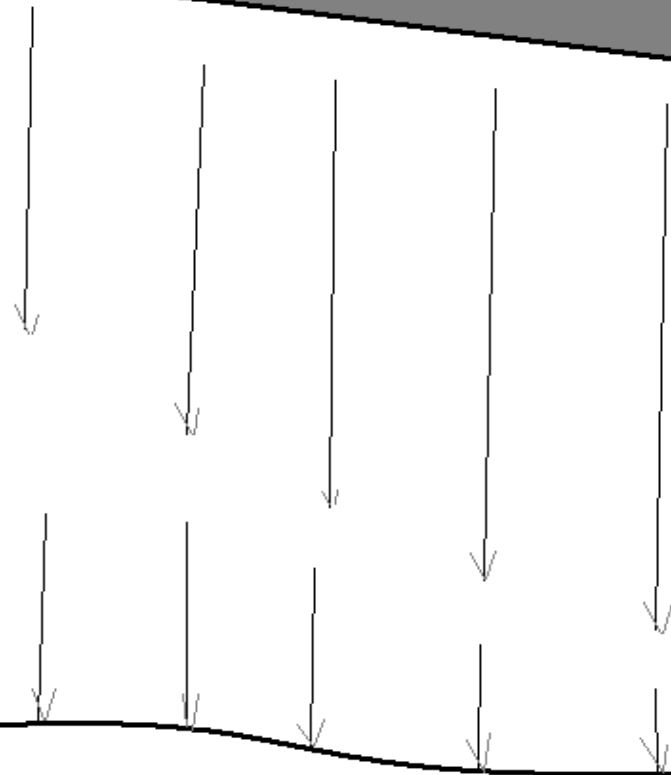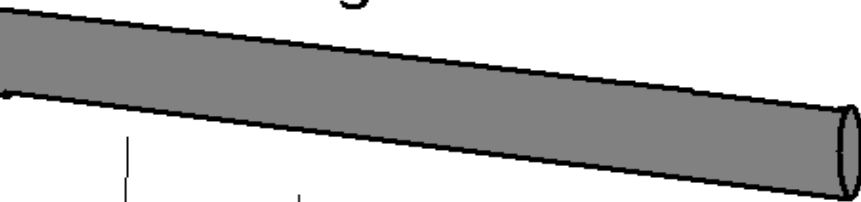

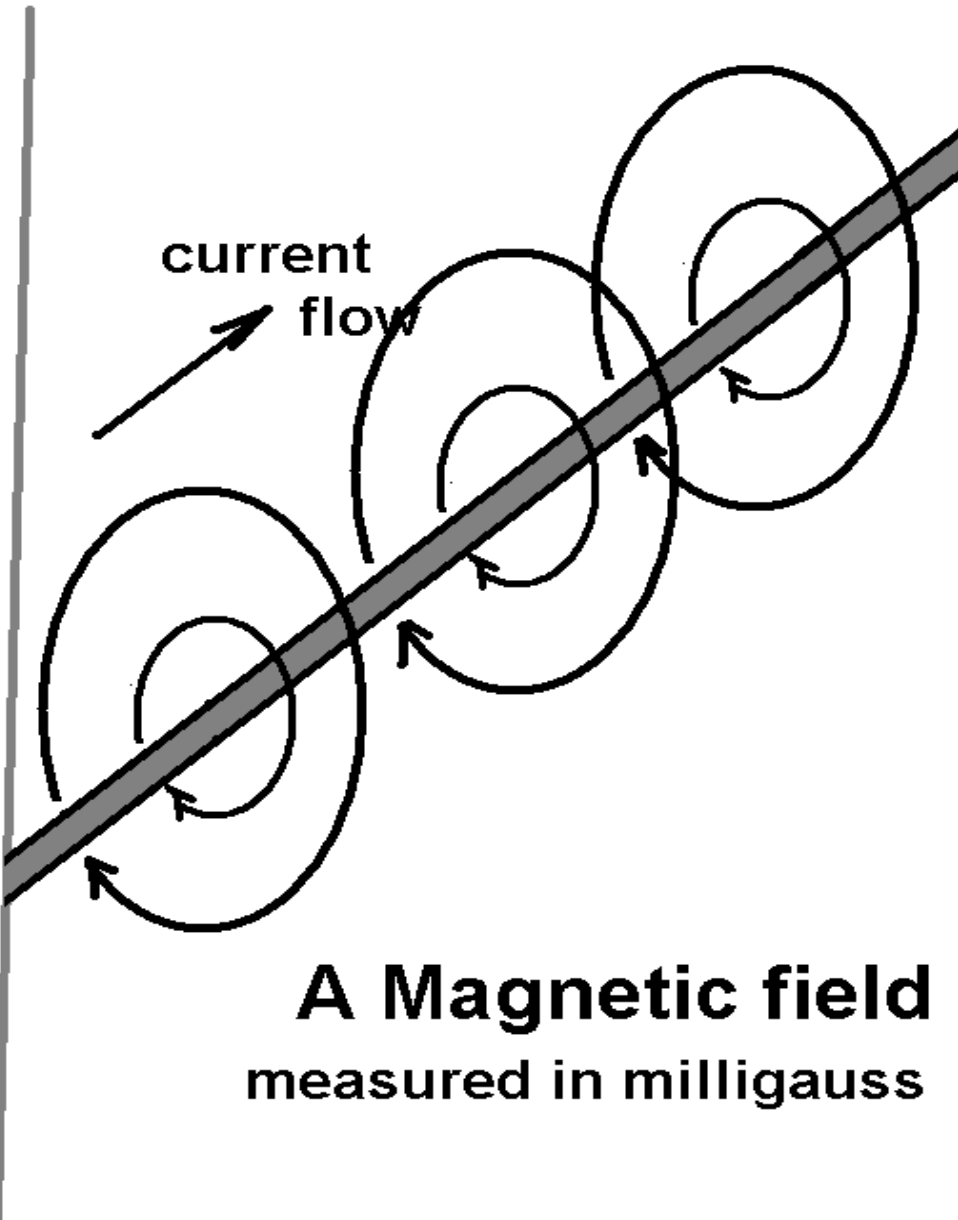**An Electric field**  
measured in volts/meter



current  
flow

**A Magnetic field**  
measured in milligauss

# What is a circuit?

- Current will only flow if one has a complete “circuit” path which allows current produced by a NON-ZERO voltage to return to its source.
- All paths have *some* level of resistance which defines the amount of current a given voltage can produce.
- Current follows all paths back to its source in inverse proportion to their resistance.

# Ohm's Law - not just a good idea, ... .. it's the law!

- $R = V / I$ ;     $I = V / R$ ;     $V = I \times R$
- **POWER,  $P = V * I$ , or  $= V^2 / R$ , or  $= I^2 * R$**
- **power (watts) not the same as energy (work measured in Joules).**
  - **POWER DELIVERED OVER TIME IS ENERGY.**
- **It is extremely important to realize the implications of voltage as either a source or as a potential difference (drop).**

# Examples:

- A voltage source of 5 volts AC rms is producing a current of 2 Amps AC rms into a resistance. What is the resistance?
- A 0.25 Ohm resistance has a current of 4 Amps AC rms running through it. What voltage drop is across this resistance?
- A voltage source of 3.6 Volts AC rms feeds a circuit with a total resistance of 1.2 Ohms, what is the current flowing?
- How much power is produced when a current of 16 Amps AC rms flows through a wire with a resistance of 0.012 Ohms?

# Answers:

- Given that  $V=5\text{v.}$  and  $I=2\text{A.}$  Then,  $R=V/I,$  so  $R=5/2=2.5$  Ohms.
- Given that  $R=0.25$  Ohm and  $I=4$  A. Then  $V=I*R,$  so  $V=0.25*4=1\text{v.}$  AC rms
- Given that  $V=3.6\text{v.}$  and  $R=1.2$  Ohms  
Then  $I=V/R,$  so  $I=3.6/1.2=3\text{A.}$  AC rms
- Given that  $I=16\text{A.}$  and  $R=0.012$  Ohm  
Then  $P=I^2*R,$  so  $P=16*16*0.012=3.072$   
Watts


# Schematic symbols




**CONDUCTOR**



**NO CONNECTION / CONNECTION**

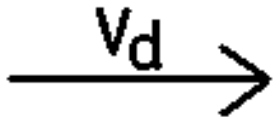


**VOLTAGE DROP**

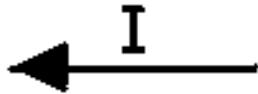

**CURRENT FLOW**




**RESISTANCE**

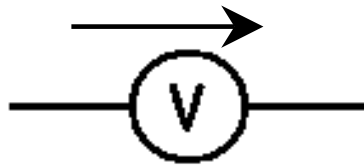


**VOLTAGE SOURCE**
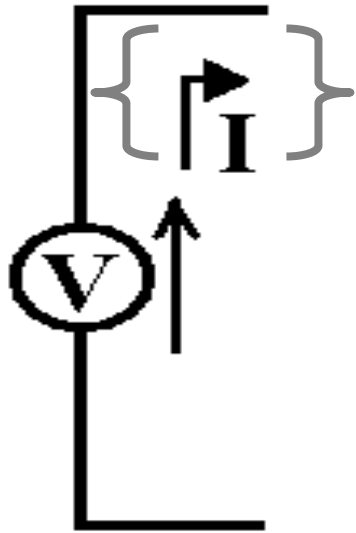
# Difference between voltage drop and voltage source.



Voltage source

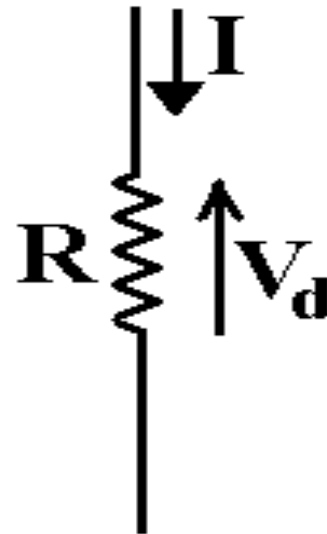

Voltage drop

# Combining resistances:

➤ **Series:** They add algebraically:

➤  $R_t = R_1 + R_2 + R_3 + \dots + R_n$

➤ **Parallel:** They add inverses to form an inverse sum:

➤  $1/R_t = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_n$

➤ **Special case of two resistors in parallel, the combined resistance is the product divided by the sum of the two resistors.**

➤  $R_t = [R_1 * R_2] / [R_1 + R_2]$

# Resistance simplification:


- **Series string: 4, 1.5, 2.3, 5.1 Ohms What is the total resistance?**
- **Parallel combination of 3.6 and 2.4 Ohm: what is the equivalent resistance?**
- **Parallel resistances: 2.4, 4.8, 6, 0.8 Ohms, what is the equivalent resistance?**
- **What is the resistance of a 4 Ohm resistor in series with a parallel combination of a 2.4 Ohm and a 1.6 Ohm resistor?**

# Resistance answers:

- Sum the resistors:  $4+1.5+2.3+5.1 = 12.9$  Ohms.
- Product over sum:  $[3.6 * 2.4] \text{ over } [3.6+2.4] = 8.64/6 = 1.44$  Ohms
- The “hard way”:  
 $(1/2.4)+(1/4.8)+(1/6)+(1/0.8) =$   
 $0.417+0.208+0.167+1.25 = 2.042$   
lastly,  $R_t = 1/2.042 = 0.49$  Ohms.
- First do the parallel pair:  
 $(2.4*1.6)/(2.4+1.6)=0.96$  Ohms in series  
with 4 Ohms gives a total of 4.96 Ohms.


# Basic circuit types

**SERIES**

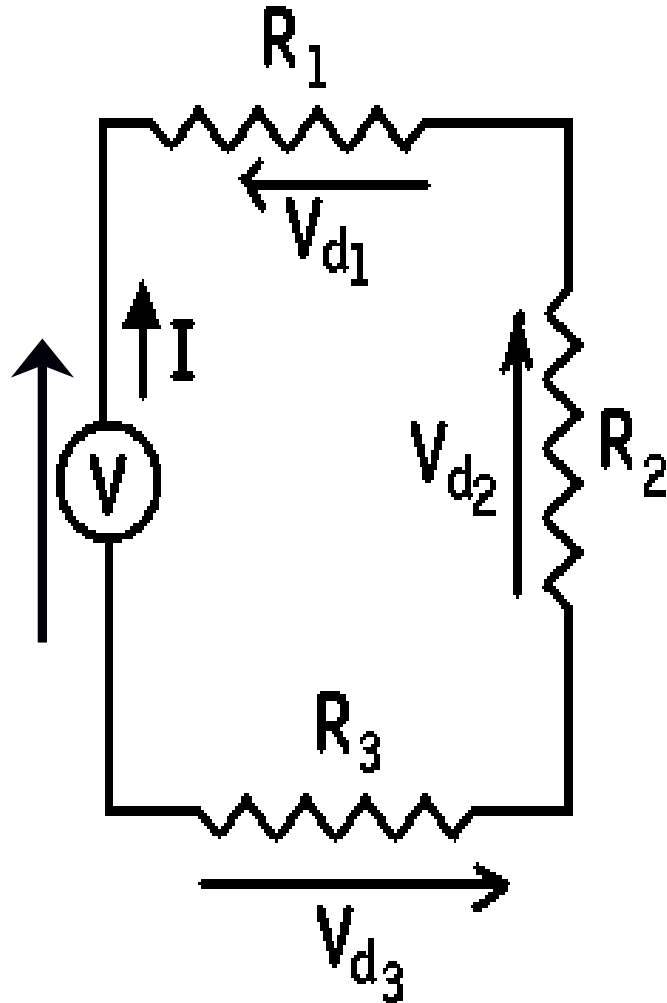

**Common current**


**PARALLEL**

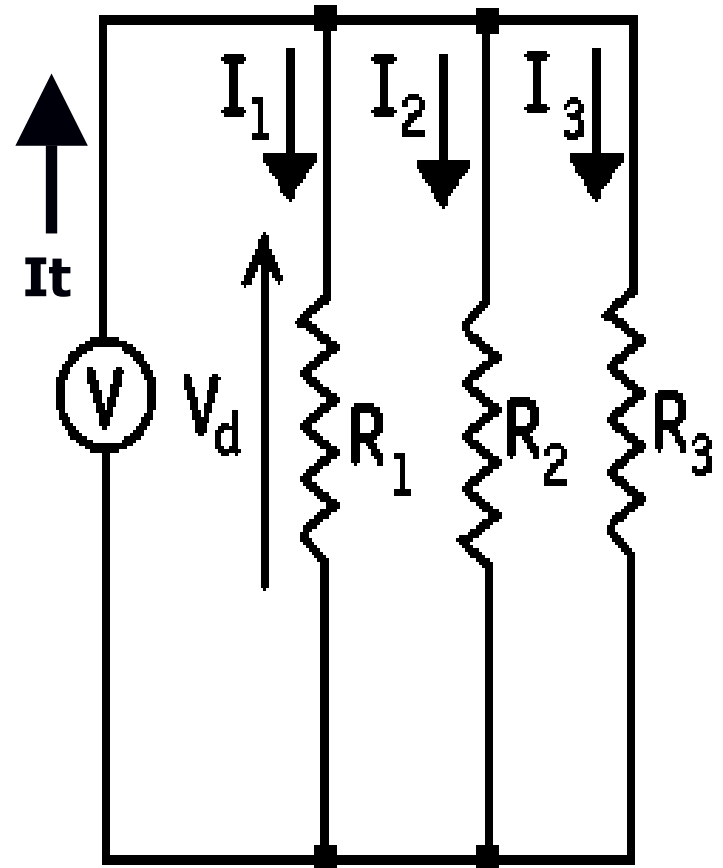

**Common voltage**

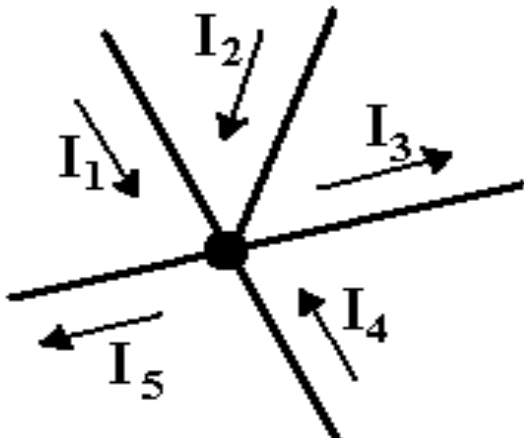
# Kirchhoff's Laws

$$\sum \mathbf{I}_{\text{point}} = \mathbf{0}$$



The sum of all currents is zero

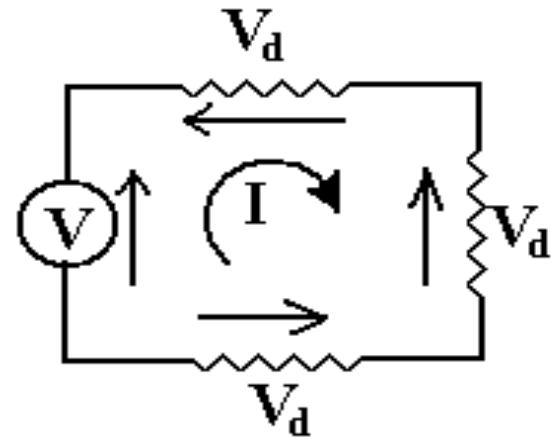
$$\sum \mathbf{V}_{\text{closed loop}} = \mathbf{0}$$



The sum of all voltage drops = the sum of all voltage sources

# 60 Hz AC waveform


**sinewave**

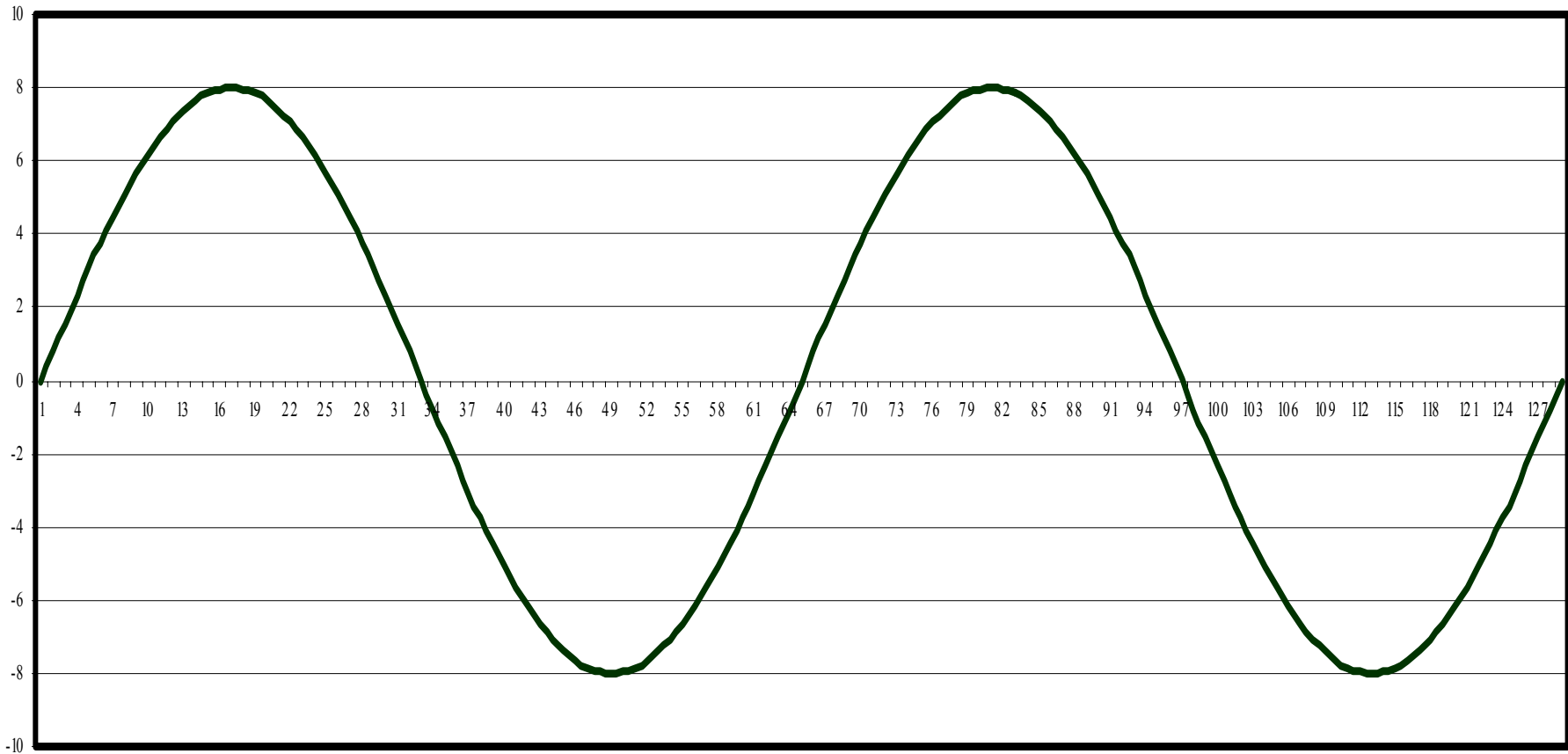


# AC measurements

- **Not polar : no permanent + and - to worry about**
- **can be expressed as a root mean square (rms) voltage or current**
- **RMS has the same “ heating value” as DC of the same level.**
- **16 Volts peak to peak is 8 Volts peak is 5.656 Volts rms (multiply by .707)**

# The nation's AC electrical system

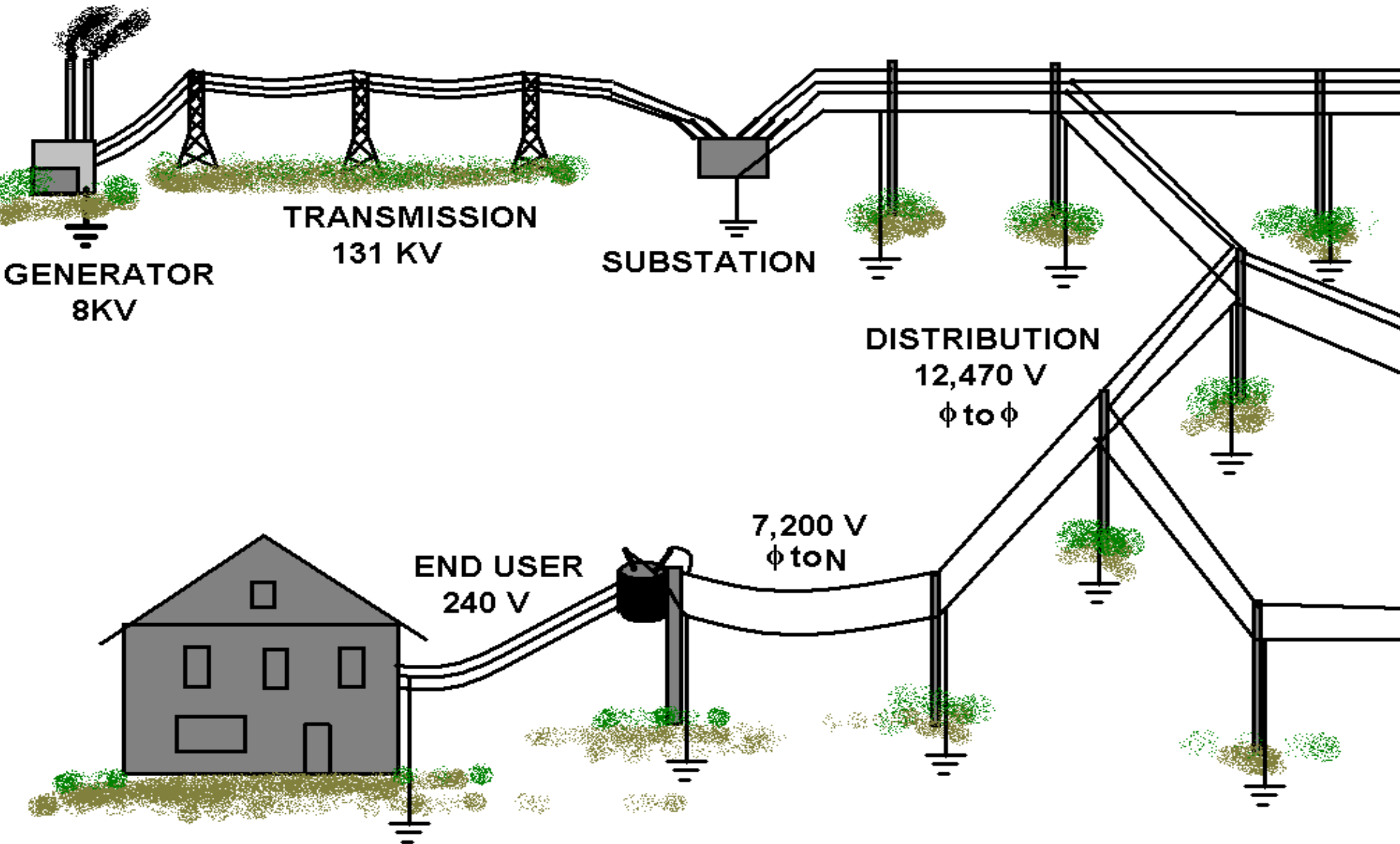

# Farm electrical system

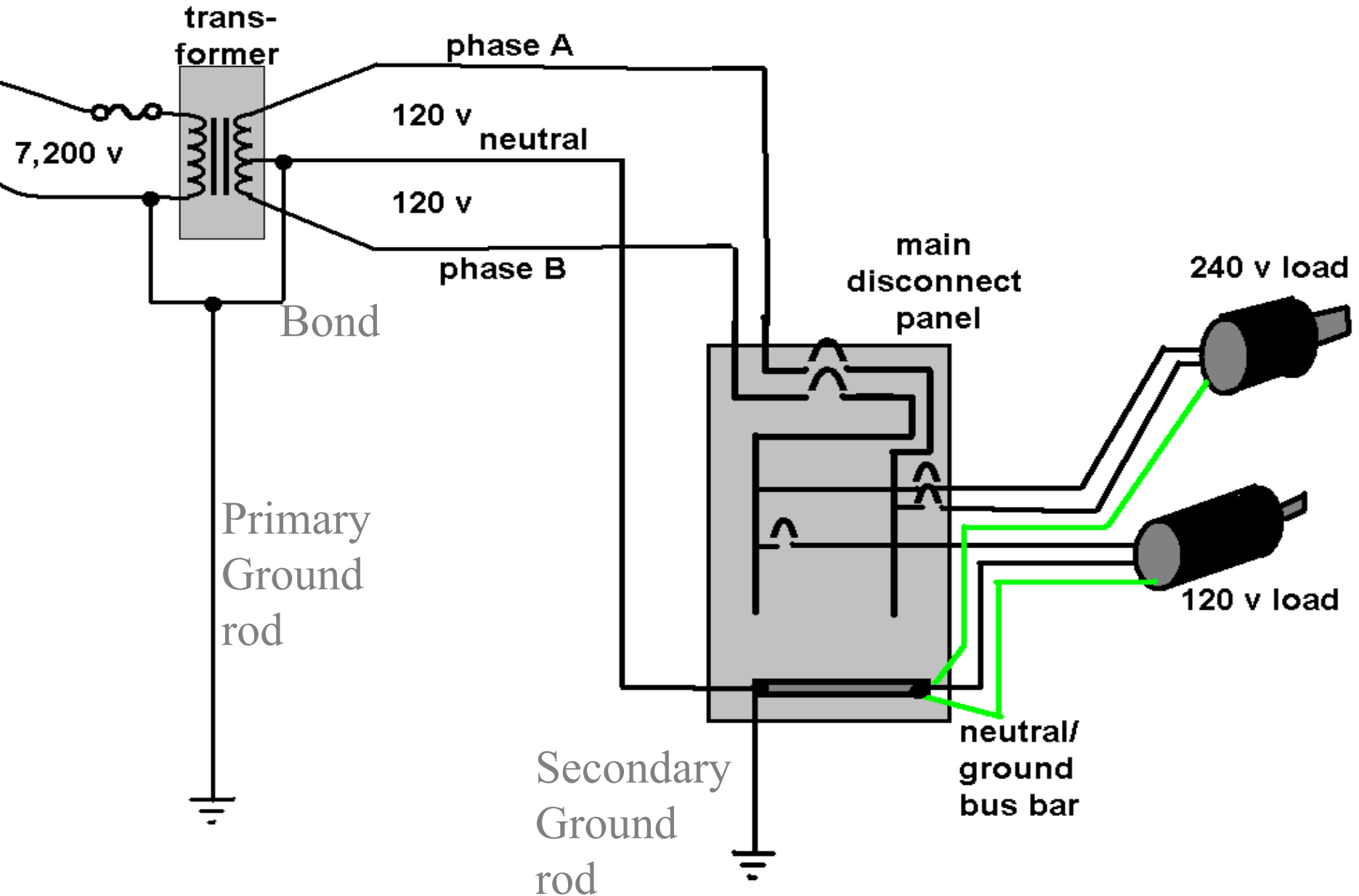

Questions???